

LAB-1 Preliminary

Please follow the instructions in the document and mail your pdf-files to the TA of your section

artunsel@gmail.com,

karahanmehmet13@gmail.com

Please name your pdf files as in the given example file:

Mehmet-Ali-Demir-111211102-lab-1-preliminary-G-3.pdf

Mehmet-Ali-Demir-111211102-lab-1-labreport-G-3.pdf

ALSO STATE YOUR SECTION in the E-MAIL, [there are 3 sections]

section-1 TA: Mehmet Karahan,

section-2 TA: Mehmet Karahan,

section-3 TA: Artun Sel.

PLEASE READ “Important Rules” section at the end of this document before submitting your document.

THE DEADLINE: Friday, October 21, 2022, 20:00.

WARNING: Any work submitted at any time within the first 24 hours following the published submission deadline will receive a penalty of 10% of the maximum amount of marks available. Any work submitted at any time between 24 hours and up to 48 hours late will receive a deduction of 20% of the marks available.

Contents

Simulation-1.....	2
Simulation-2.....	3
Simulation-3.....	4
Simulation-4.....	4
Simulation-5.....	4
Simulation-6.....	5
Simulation-7.....	5
Simulation-8.....	6
Simulation-9.....	6
Simulation-10.....	7

Simulation-1

In this study, the circuit given below is to be simulated. There are 3 resistors, 1 capacitor, 1 op-amp and 1 voltage source.

Then, the “reference voltage” and “output voltage” signals are to be measured.

[You can use any circuit-simulation-program that you want]

Here, as an example “LT-spice” has been used and reference voltage and output voltage have been measured.

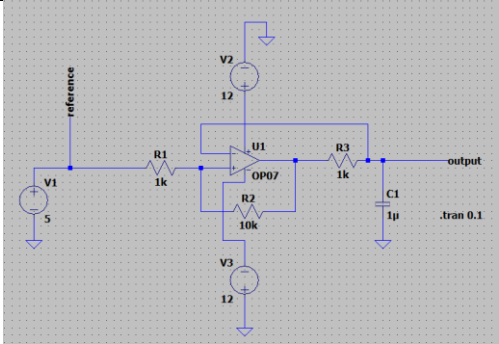
	<p>The circuit parameters are given in the table below.</p> <p style="text-align: center;">Table-1: The circuit parameters</p> <table border="1" style="width: 100%; border-collapse: collapse; margin-top: 10px;"> <thead> <tr> <th style="text-align: center;">The parameter</th> <th style="text-align: center;">Value</th> </tr> </thead> <tbody> <tr> <td style="text-align: center;">R_1</td> <td style="text-align: center;">$1k\Omega$</td> </tr> <tr> <td style="text-align: center;">R_2</td> <td style="text-align: center;">$10k\Omega$</td> </tr> <tr> <td style="text-align: center;">R_3</td> <td style="text-align: center;">$1k\Omega$</td> </tr> <tr> <td style="text-align: center;">C_1</td> <td style="text-align: center;">$1\mu F$</td> </tr> <tr> <td style="text-align: center;">Op-amp V^+</td> <td style="text-align: center;">$+12V$</td> </tr> <tr> <td style="text-align: center;">Op-amp V^-</td> <td style="text-align: center;">$-12V$</td> </tr> <tr> <td style="text-align: center;">Op-amp</td> <td style="text-align: center;">Type:741</td> </tr> </tbody> </table>	The parameter	Value	R_1	$1k\Omega$	R_2	$10k\Omega$	R_3	$1k\Omega$	C_1	$1\mu F$	Op-amp V^+	$+12V$	Op-amp V^-	$-12V$	Op-amp	Type:741
The parameter	Value																
R_1	$1k\Omega$																
R_2	$10k\Omega$																
R_3	$1k\Omega$																
C_1	$1\mu F$																
Op-amp V^+	$+12V$																
Op-amp V^-	$-12V$																
Op-amp	Type:741																

Figure 1: op-amp Circuit

Use the circuit parameters as given in Table-1. The other parameters for this simulation are given in the table-2 below.

Table 2: Circuit Simulation Parameters

The parameter	Value
$V_{reference}$	$+5V$
<i>simulation duration</i>	$100ms$

Then measure, “reference voltage” and “output voltage”.

[The plot must be clearly visible, THE BACKGROUND OF THE PLOT MUST BE WHITE!!!]

The simulation output must be the plot given below.

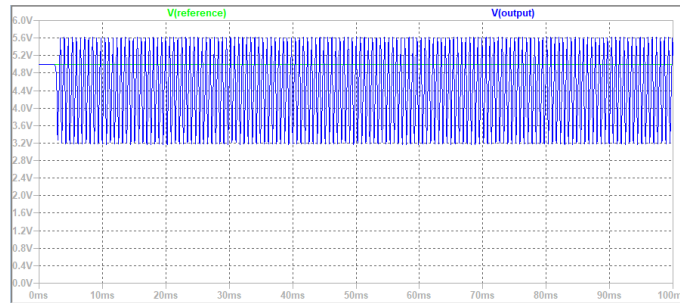


Figure 2: Spice Simulation Output

As an example, the same circuit has been simulated by using matlab-simulink-simscape-electronics.

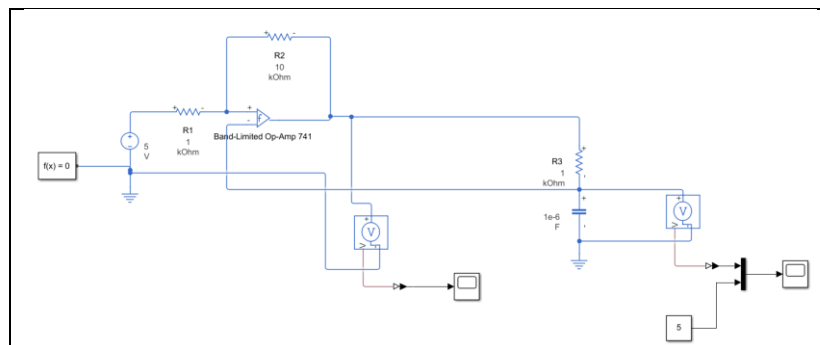


Figure 3: Matlab-simulink-simscape-electronics

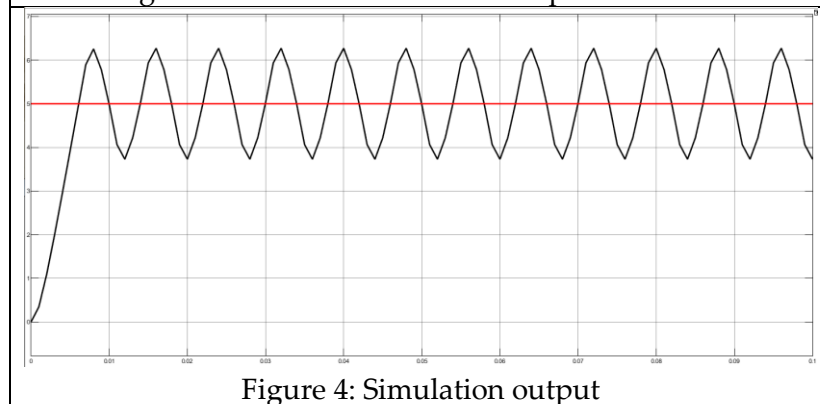


Figure 4: Simulation output

AGAIN: [You can use any circuit-simulation-program that you are familiar with!]

Simulation-2

Use the circuit parameters as given in Table-1. The other parameters for this simulation are given in the table below.

Table 3: Circuit Simulation Parameters

The parameter	Value
<i>V reference</i>	<i>square wave signal {0V, 5V}, 10Hz</i>
<i>simulation duration</i>	1s

Then measure, “reference voltage” and “output voltage”.

[The plot must be clearly visible, THE BACKGROUND OF THE PLOT MUST BE WHITE!!!]

Simulation-3

Use the circuit parameters as given in Table-1. The other parameters for this simulation are given in the table below.

Table 4: Circuit Simulation Parameters

The parameter	Value
<i>V reference</i>	<i>sine wave signal {peak – to – peak voltage: 5V}, 10Hz</i>
<i>simulation duration</i>	1s

Then measure, “reference voltage” and “output voltage”.

[The plot must be clearly visible, THE BACKGROUND OF THE PLOT MUST BE WHITE!!!]

Simulation-4

Use the circuit parameters as given in Table-1. The other parameters for this simulation are given in the table below.

Table 5: Circuit Simulation Parameters

The parameter	Value
<i>V reference</i>	<i>sine wave signal {peak – to – peak voltage: 5V}, 20Hz</i>
<i>simulation duration</i>	1s

Then measure, “reference voltage” and “output voltage”.

[The plot must be clearly visible, THE BACKGROUND OF THE PLOT MUST BE WHITE!!!]

Simulation-5

Use the circuit parameters as given in Table-1. The other parameters for this simulation are given in the table below.

Table 6: Circuit Simulation Parameters


The parameter	Value
$V_{reference}$	<i>sine wave signal</i> {peak – to – peak voltage: 5V}, 100Hz
simulation duration	1s

Then measure, “reference voltage” and “output voltage”.

[The plot must be clearly visible, THE BACKGROUND OF THE PLOT MUST BE WHITE!!!]

Simulation-6

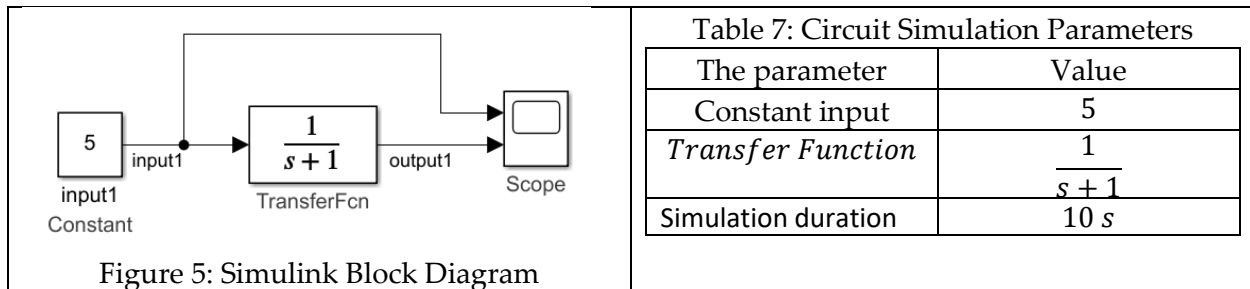Using **MATLAB-Simulink**, simulate the given system below.



Then measure, “input1 signal” and “output1-signal”.

[The plot must be clearly visible, THE BACKGROUND OF THE PLOT MUST BE WHITE!!!]

The simulation output must be the plot given below.


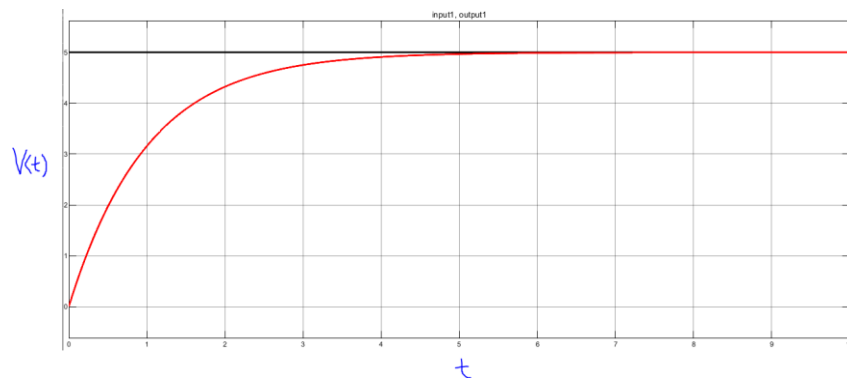


Figure 6: Simulink simulation output

Simulation-7

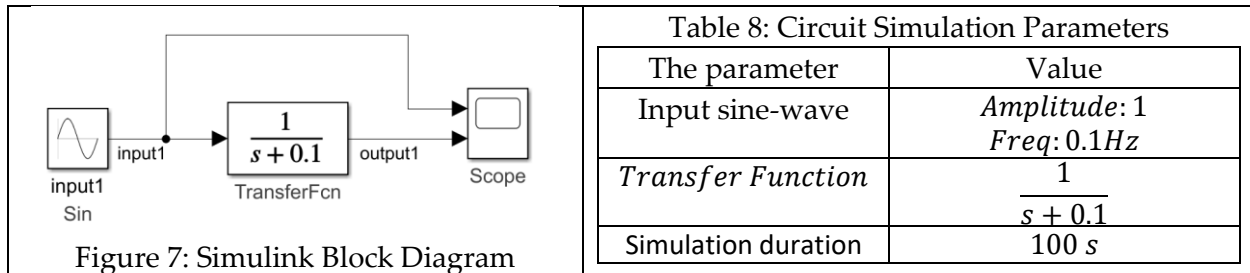Using **MATLAB-Simulink**, simulate the given system below.




The parameter	Value
Input sine-wave	<i>Amplitude: 1</i> <i>Freq: 0.1Hz</i>
<i>Transfer Function</i>	$\frac{1}{s + 0.1}$
Simulation duration	100 s

Then measure, “input1 signal” and “output1-signal”.


[The plot must be clearly visible, THE BACKGROUND OF THE PLOT MUST BE WHITE!!!]

Simulation-8

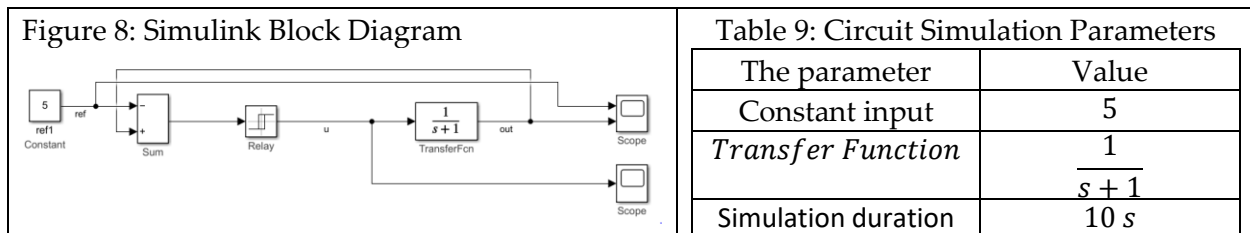Using **MATLAB-Simulink**, simulate the given system below.



The parameter	Value
Constant input	5
<i>Transfer Function</i>	$\frac{1}{s + 1}$
Simulation duration	10 s

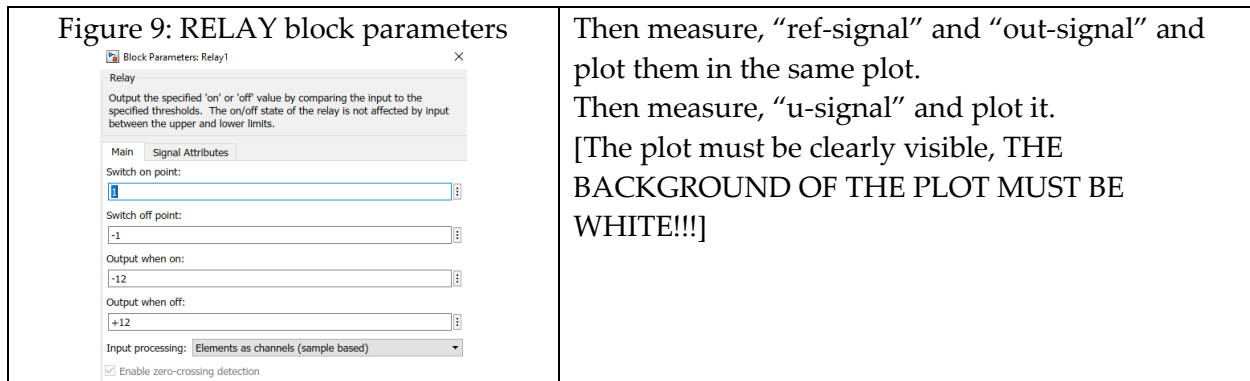


Then measure, “ref-signal” and “out-signal” and plot them in the same plot.

Then measure, “u-signal” and plot it.

[The plot must be clearly visible, THE BACKGROUND OF THE PLOT MUST BE WHITE!!!]

Simulation-9

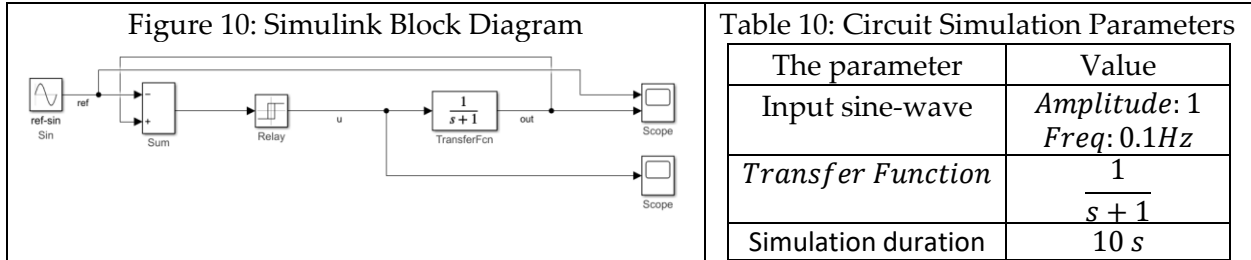Using **MATLAB-Simulink**, simulate the given system below.




Then measure, “ref-signal” and “out-signal” and plot them in the same plot.

Then measure, “u-signal” and plot it.

[The plot must be clearly visible, THE BACKGROUND OF THE PLOT MUST BE WHITE!!!]

Simulation-10

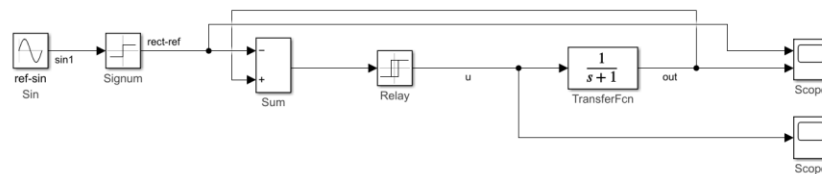Using **MATLAB-Simulink**, simulate the given system below.



The parameter	Value
Reference signal [rect-ref]	$sgn(\sin(2\pi(0.1)t))$
<i>Transfer Function</i>	$\frac{1}{s + 1}$
Simulation duration	10 s

[The RELAY block parameters are given in Figure 10.]

Then measure, “rect-ref-signal” and “out-signal” and plot them in the same plot.

Then measure, “u-signal” and plot it.

[The plot must be clearly visible, THE BACKGROUND OF THE PLOT MUST BE WHITE!!!]

Important Rules

The following is the list of the rules that must be followed. The failure of following the rules listed below will be resulted in point-deduction as stated in the table.

No.	Rule	Corresponding point-deduction for the failure of following the rule
01	The document must be mailed to TA of the section	5 pt.
02	The pdf file must be named as stated at the top of the document	5 pt.
03	The file must be in pdf format	5 pt.
04	Section-name must be stated in the mail that is to be sent to submit the lab-report or preliminary document	5 pt.
05	The deadline must be met.	10 pt. for each day after the deadline
06	The file must be prepared in digital form. MSword or Latex must be used.	5 pt.
07	All plots must be on a white background and the lines must be clearly visible. The names of the signals in the plot must be stated [either by using legend or by using appropriate Figure Naming such as "Figure 1: (red) input signal, (blue) output signal"]	3 pt.
08	All figures must be numbered.	3 pt.
09	All tables must be numbered.	3 pt.
10	All equations must be numbered.	3 pt.
11	Reference must be added. Only books are allowed. Do not use internet sources. Example references: [1] "Modern Control Engineering 5 th Ed", Ogata K., 2010, Prentice Hall [2] "Linear Systems Theory 2 nd Ed", Hespanha J., 2018, Princeton Press	3 pt.
12	Font style must be consistent. Times-New-Roman or Palatino-Linotype must be used. Font size must be 11.	3 pt.

